

Program: Diploma in Information Technology
/Computer Engineering

Year/Part: I/II

Subject: Logic Circuits

www.rjankc.com.np

Full Marks: 60

Pass Marks: 24

Time: 3 hrs

Candidates are required to give their answers in their own words as far as practicable.
The figures in the margin indicates full marks.

Attempt Any Five (5) Questions.

1.	a] Define signal. Differentiate between analog and digital signal with suitable example.	[2+4=6]
	b] Convert the following number system. i] $(2564.87D)_{16} = (?)_2$ ii] $(4432.123)_8 = (?)_{16}$ iii] $(111101010 * 11010)_2$ iv] $(1101001.110)_2 / (110)_2$	[1×4=4]
	c] Subtract the following $(11101010)_2$ from $(111110000)_2$ using 2's Complement.	[2]
2.	a] Explain about AND and OR gate with necessary truth table, symbol and logical expression.	[3+3]
	b] Define Universal gate. Explain how NOR gate operate as Basic gate with necessary realization technique.	[1+5]
3.	a] Simplify the following expression using K-map. $\Sigma F(A,B,C,D) = \Sigma m(0,1,3,4,7,8,12,15) \Sigma d(2,5,6,14)$	[6]
	b] Define adder. Explain the operation of Full adder with clear diagram and truth table.	[1+5]
4.	a] Define Encoder. Design BCD to decimal decoder with clear circuit diagram and truth table.	[1+5]
	b] Design 8:1 Multiplexer with clear circuit diagram and truth table.	[6]
5.	a] Define Flip-flop. Explain the operation of JK flip flop with necessary diagram and truth table.	[1+5]
	b] Define counter. Explain the operation of ripple counter with clear diagram.	[1+5]

6.	Write short notes on: (Any Four)	[4×3=12]
	a] LCD Display b] SISO shift register c] Gray code d] De Morgan's theorem e] Demultiplexer	

Good Luck!

For Educational Materials

Don't Forget to visit:

<http://www.rjankc.com.np>

Direct Contact: +977-9855080226/9845080226